

Digital Electronics (EC0319)

(K map ,tabulation Method & SOP,POS Question Bank)

- 1) Obtain the simplified expressions & Find out F & F' in sum of products and product of sum for the Following Boolean functions: $F(A,B,C,D,E) = \Sigma(0,1,4,5,16,17,21,25,29)$
- 2) Simplify the Boolean function using kmap :
 - (1) $F(w,x,y,z) = \Sigma m(0,1,2,4,5, 12,13,)$
 - (2) $F = A'B'D' + A'CD + A'BC$ $d = A'BC'D + ACD + AB'D'$ Where "d " indicates Don't care Conditions
- 3) Simplify the Boolean function using k-map & implement the expression using NOR & NAND logic. $F(w,x,y,z) = \Sigma m(0,1,2,4,5, 12,13)$
- 4) Obtain the simplified expressions for the Following Boolean functions & Implement this logic into AOI logic:
 $F(A,B,C,D,E) = \Pi M(0,1,2,4,7,8,12,14,15,16,17,18,20,24,28,30,31)$
- 5) Reduce the following expression in SOP form using mapping and implement the minimal expression using NAND and NOR logic $F = \Sigma m(0,2,3,10,11,12,13,16,17,18,19,20,21,26,27)$
- 6) Simplify the following Boolean expression using K-map. Implement same using NAND gates only. $F(a,b,c,d) = \Sigma m(0,3,6,7,11,14,15)$
- 7) Minimize the following expression using K-map and implement the minimal expression using NAND and NOR logic $F(A,B,C,D) = \Pi M(4,5,7,12,14,15) + \Sigma d(3,8,10)$
- 8) Minimize the following expression using K-map: $F = \Pi M(2,3,7,8,9,10,11,12,16,17,18,19,20,21,23,26,27)$
- 9) Obtain the simplified expressions in sum of products for the Following Boolean function, implement this logic into AOI logic and implement the minimal expression using NAND and NOR logic.: $(A,B,C,D,E) = \Pi M(0,1,4,5,16,17,21,25,29)$
- 10) Minimize the following expression using K-map and implement this logic into AOI logic and implement the minimal expression using NAND and NOR logic.:
- 11) $F(A,B,C,D) = \Sigma m(1,3,7,11,15) + \Sigma d(0,2,5)$

- 12) Obtain the simplified expressions using k-map. $F(A,B,C,D,E) = \sum m(0,1,2,4,7,8,12,14,15,16,17,18,20,24,28,30,31)$
- 13) Obtain the simplified expressions for the Following Boolean functions:
 $F(A,B,C,D,E) = \prod M(0,1,4,5,16,17,21,25,29)$
- 14) Expand $F(A,B,C,D) = A + BC' + ABD' + ABCD$ to Maxterm & Minterm .
- 15) Obtain the product of sum of the function: $A(B' + A)B$
- 16) Expand $A(A' + B)(A' + B + C')$ to Maxterm & Minterm
- 17) Obtain the simplified expressions in sum of products for the Following Boolean functions & Implement it into Kmap : $A'B'CE' + A'B'C'D' + B'D'E' + B'CD$.
- 18) Obtain the simplified expressions in SOP form for the following Boolean function & Implement it into Kmap: $F(A, B, C, D) = ABD + A'C'D' + A'B + A'CD' + AB'D$
- 19) Obtain minimal expression for $\sum m(1,2,3,5,6,7,8,9,12,13,15)$ using tabular method.
- 20) Minimize the following expression $\sum m(0,12,8,9,15,17,21,24,25,27,31)$ using tabular method.