

III Sem
Digital Electronics
shift registers

1. Explain following registers with necessary diagram
 - I. 4 bit Serial-In Serial-Out Shift Register (with D flip flop , J-K flip flop ,S-R flip flop)
 - II. 4 bit Serial-In parallel -Out Shift Register
 - III. Parallel-In serial-Out Shift Register
 - IV. 4 bit Parallel-In Parallel-Out Shift Register.